





An MoE Govt of India Initiative


Differentiator using Opamp

INSTRUCTION

OSCILLOSCOPE

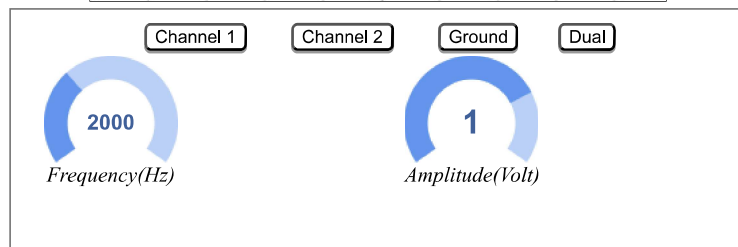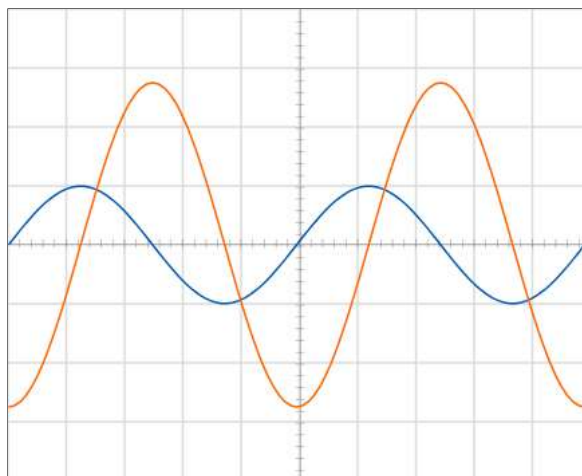Virtual Oscilloscope Tutorial : [Virtual Oscilloscope Tutorial](#)

CIRCUIT

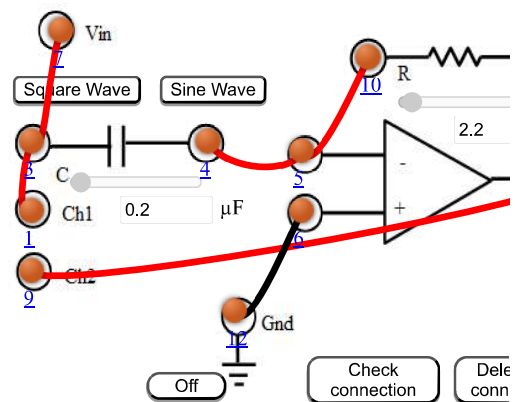

CONTROLS

