
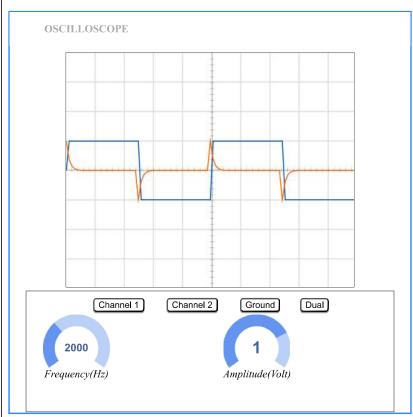



Differentiator using Opamp

INSTRUCTION

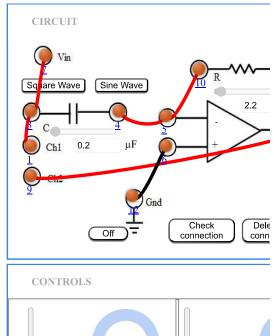

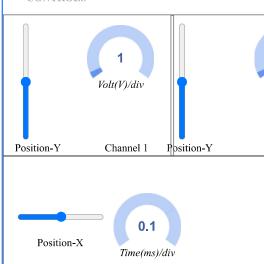Virtual Oscilloscope Tutorial : Virtual Oscilloscope Tutorial





Copyright © 2011 Indian Institute of Technology Kharagpur, <u>Licensing Terms</u>